#### **EE2011 Computer Organization**


Lecture 7\_2: The Processor – Datapath Examples

Wen-Yen Lin, Ph.D.
Department of Electrical Engineering
Chang Gung University
Email: wylin@mail.cgu.edu.tw

May 2022



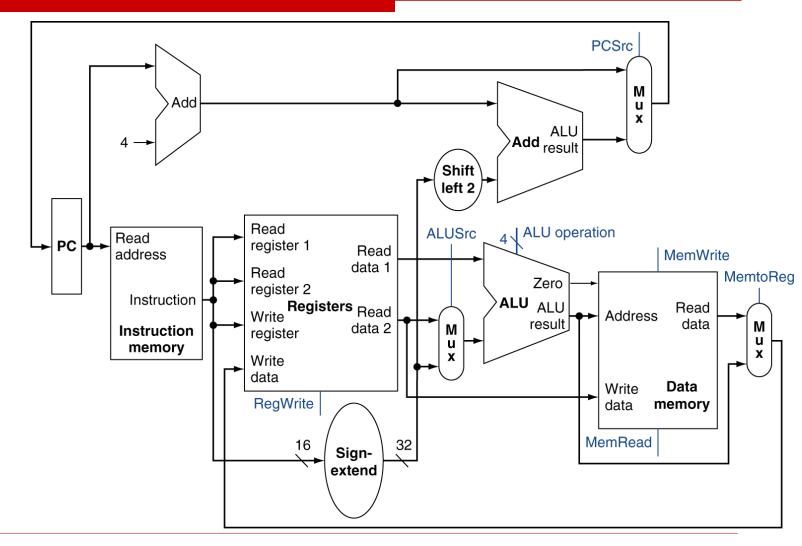
# Putting All Together for the Datapath (Fig. 4.11)





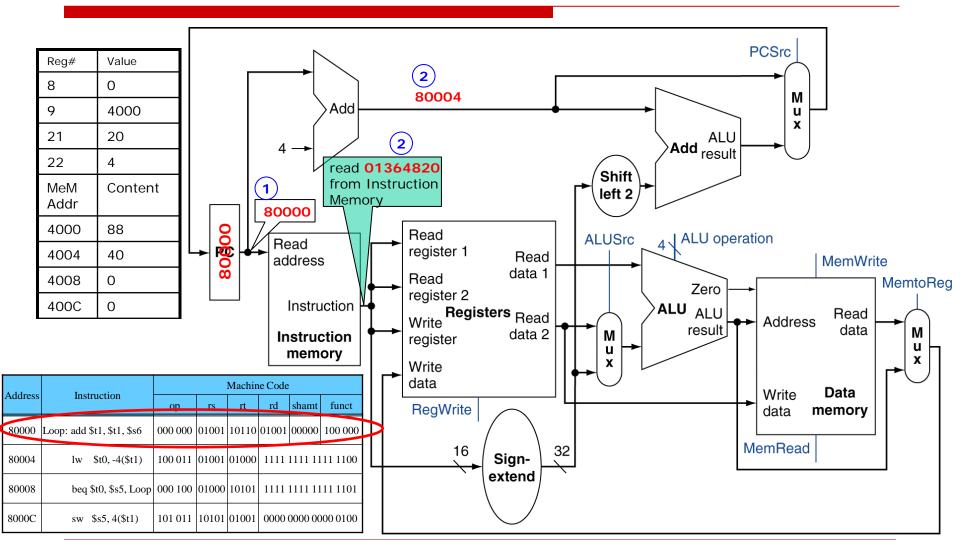
#### How data flow through datapath Example: R-type Instruction: add (I-Fetch)





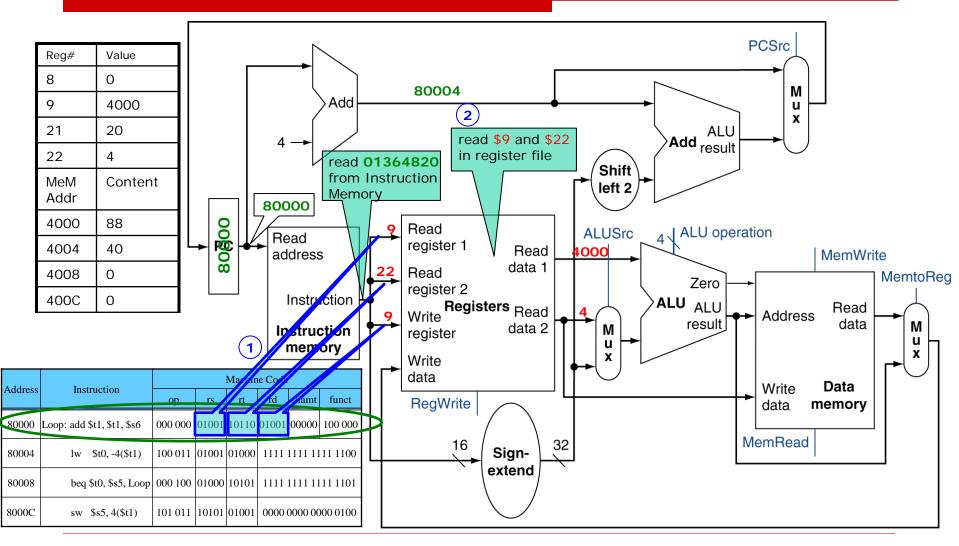
#### How data flow through datapath Example: R-type Instruction: add (R-Read)





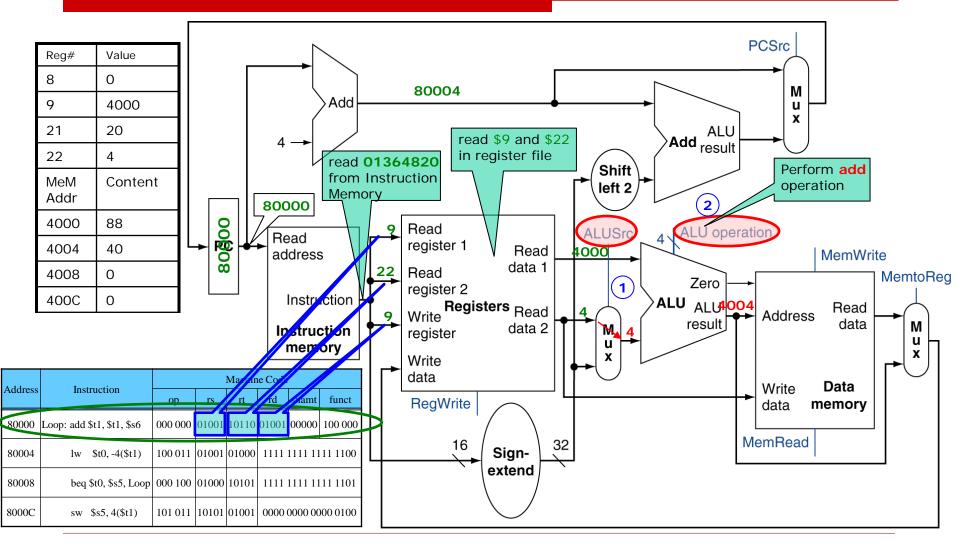
#### How data flow through datapath Example: R-type Instruction: add (EXE)





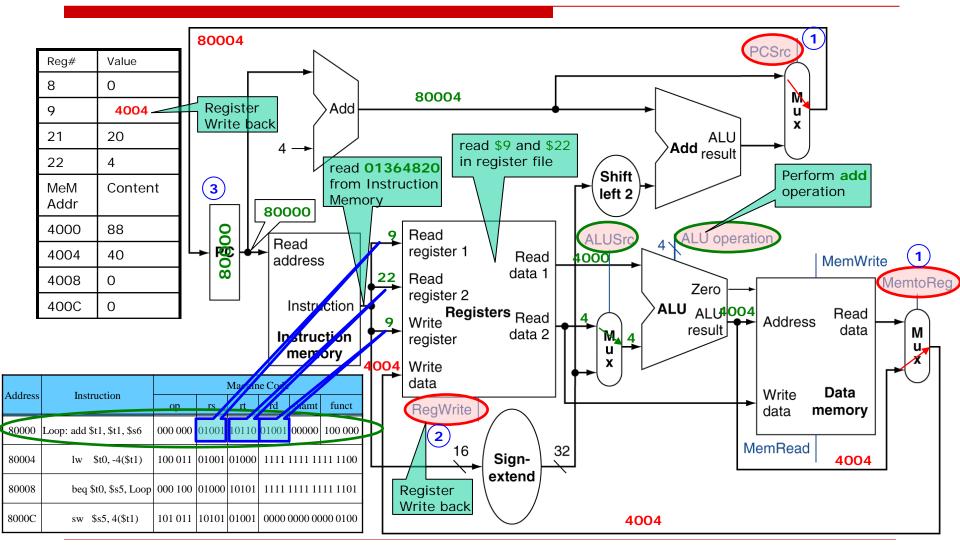
#### How data flow through datapath Example: R-type Instruction: add (WB)



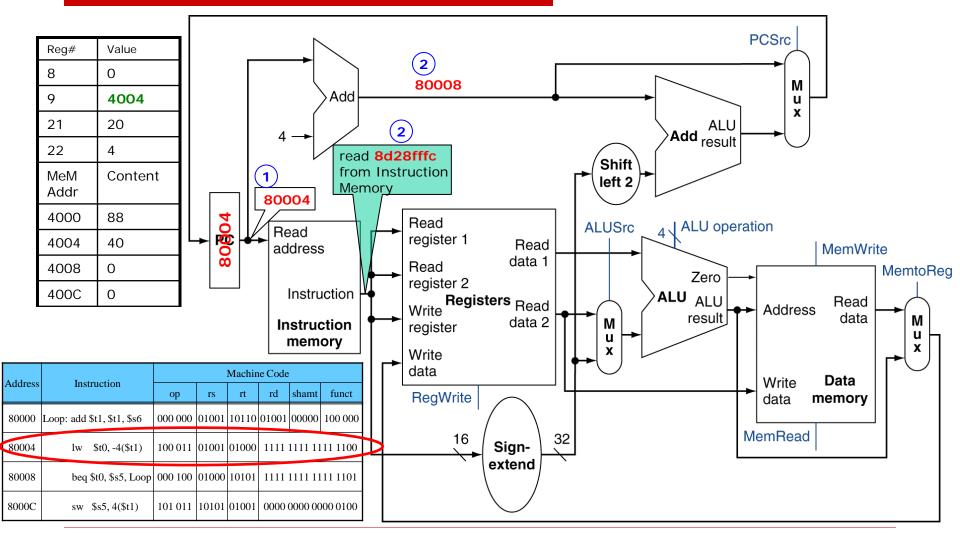
### How data flow through datapath Example: I-type Instruction: Iw (I-Fetch)




#### Parallel Processing and SoC Lab Chang Gung University
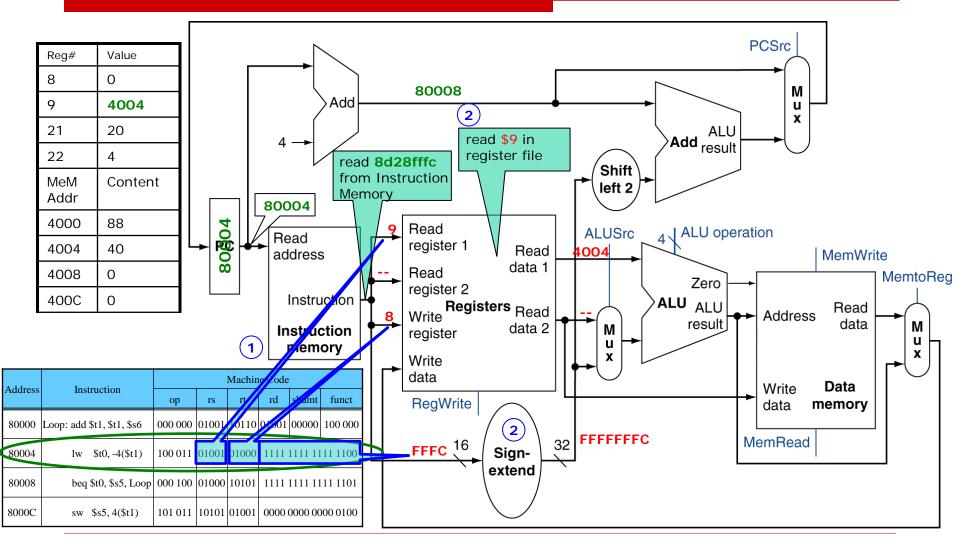
#### How data flow through datapath Example: I-type Instruction: Iw (R-Read)





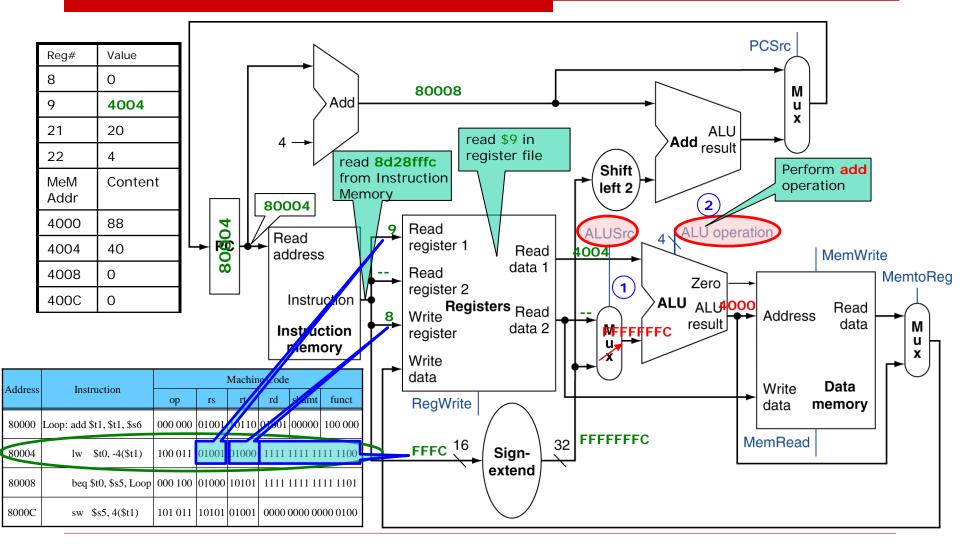
### How data flow through datapath Example: I-type Instruction: Iw (EXE)





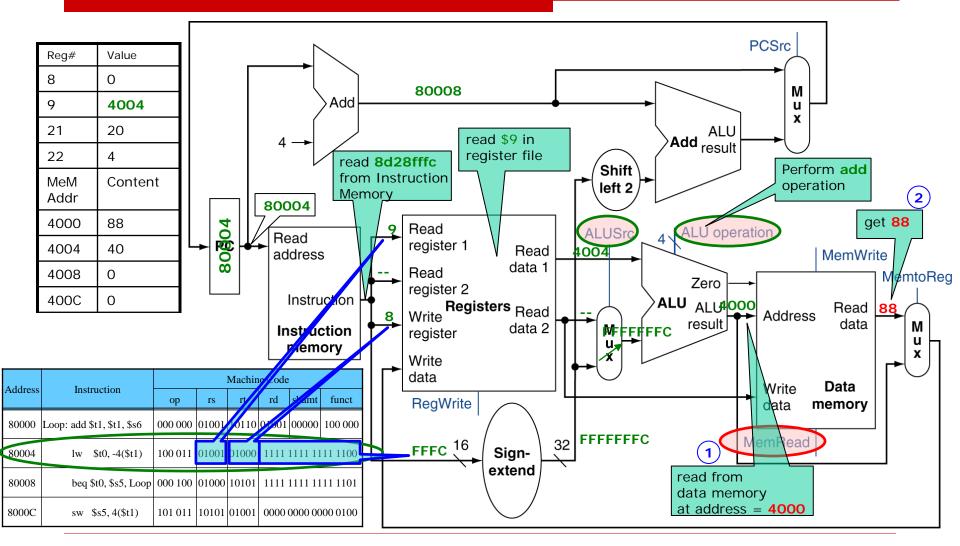
#### How data flow through datapath Example: I-type Instruction: Iw (MEM)





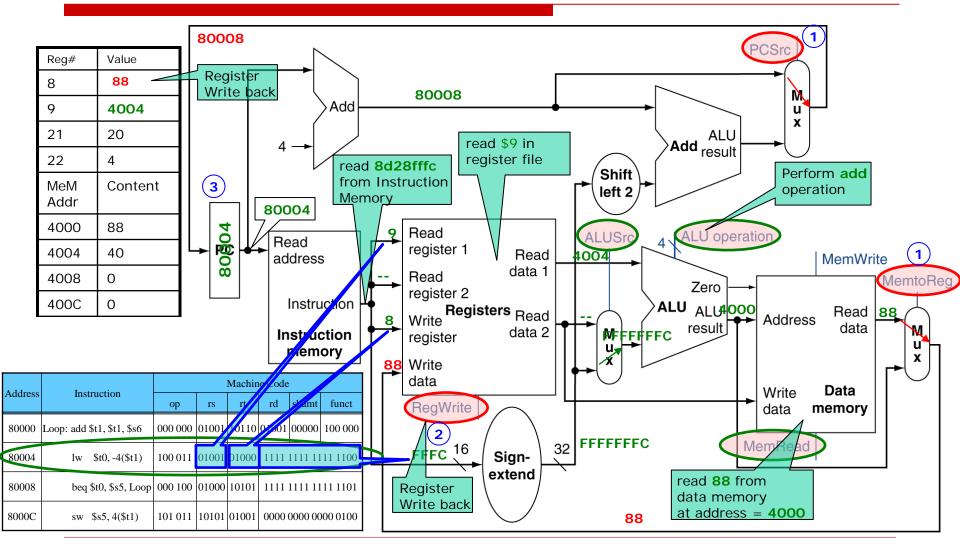
### How data flow through datapath Example: I-type Instruction: Iw (WB)





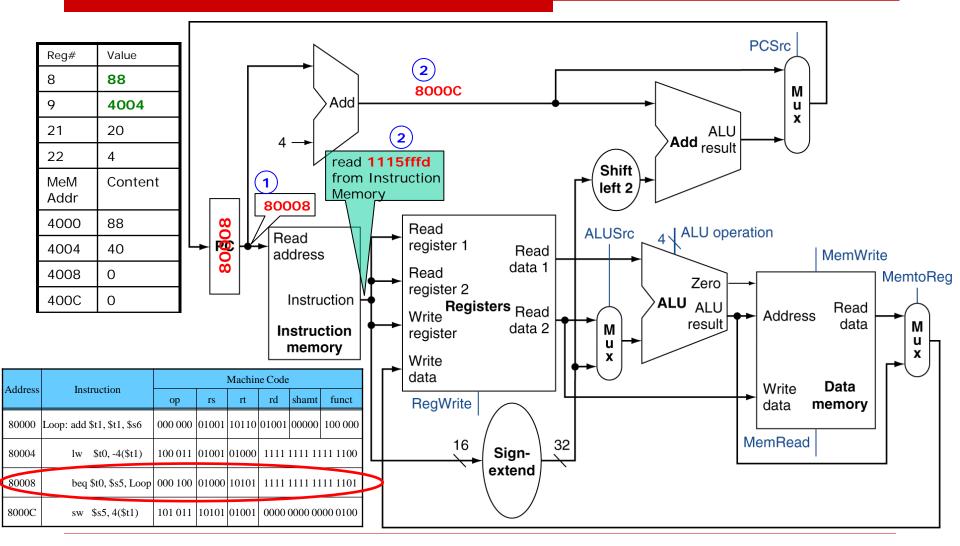
#### How data flow through datapath Example: I-type Instruction: beq (I-Fetch)




#### Parallel Processing and SoC Lab Chang Gung University
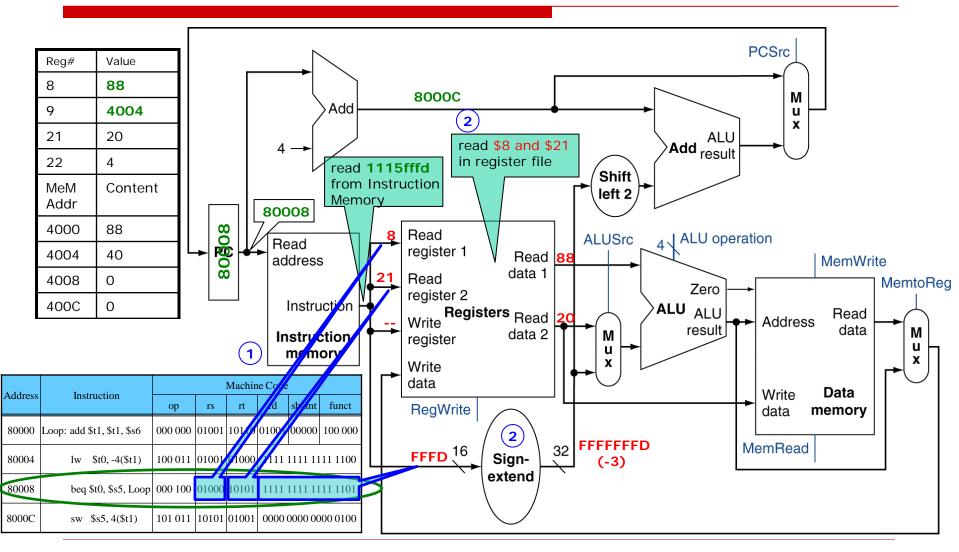
#### How data flow through datapath Example: I-type Instruction: beq (R-Read)




#### How data flow through datapath

Example: I-type Instruction: beq (EXE)

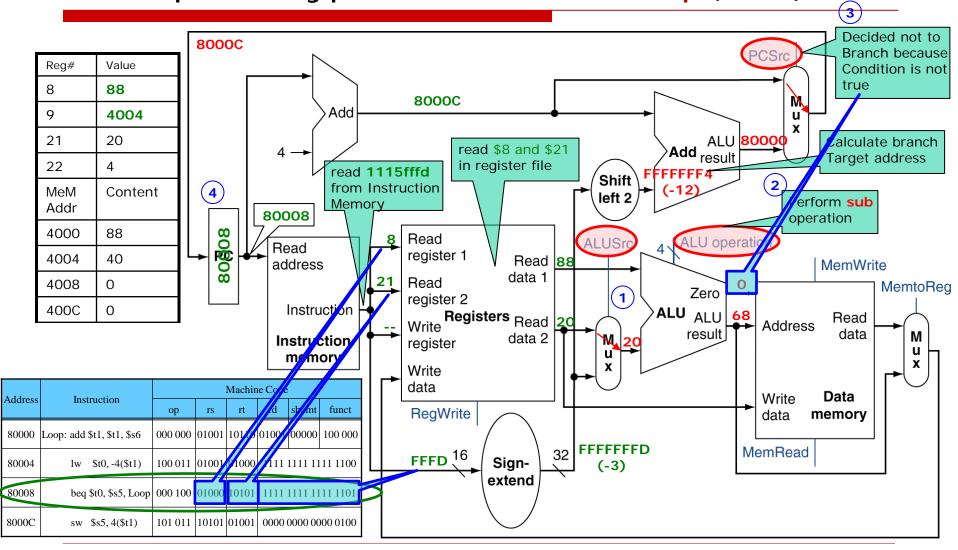



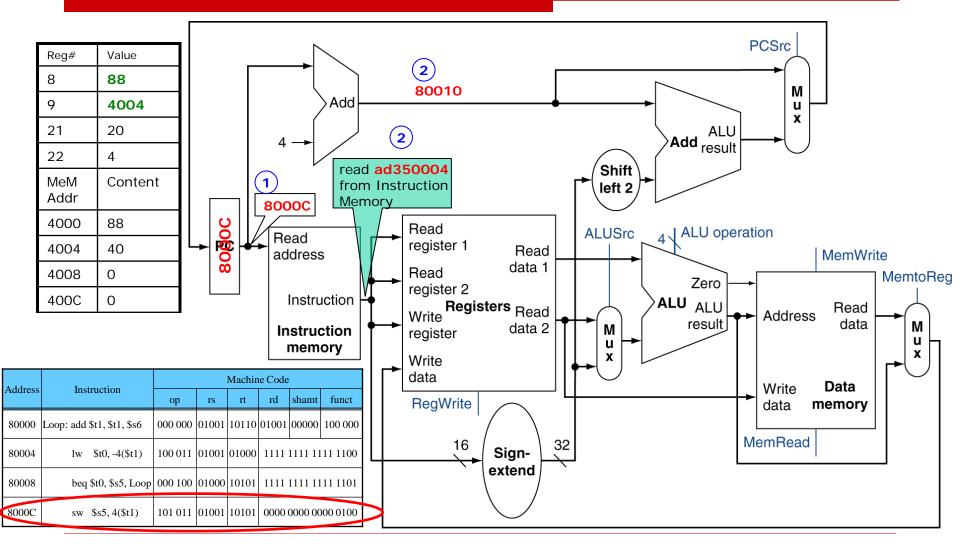
#### How data flow through datapath Example: I-type Instruction: sw (I-Fetch)





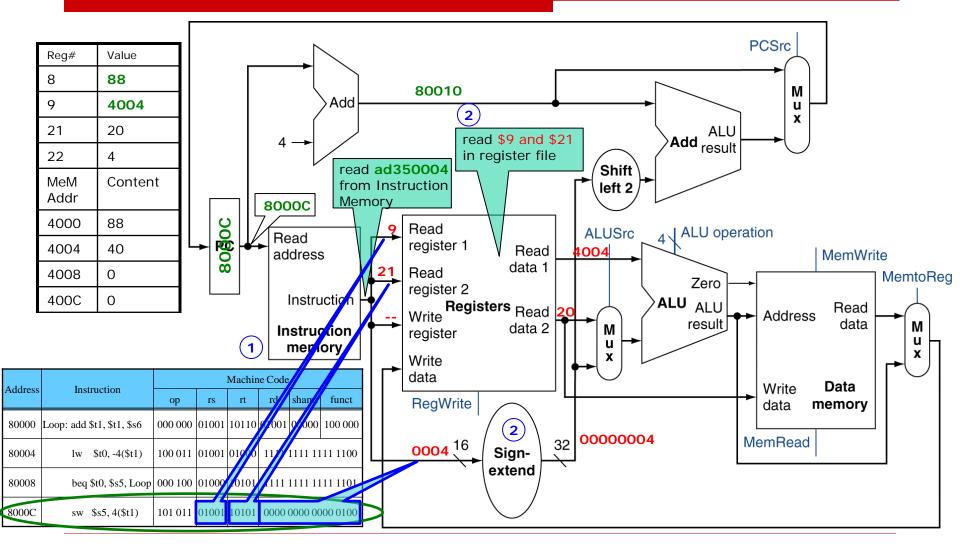
#### How data flow through datapath Example: I-type Instruction: sw (R-Read)





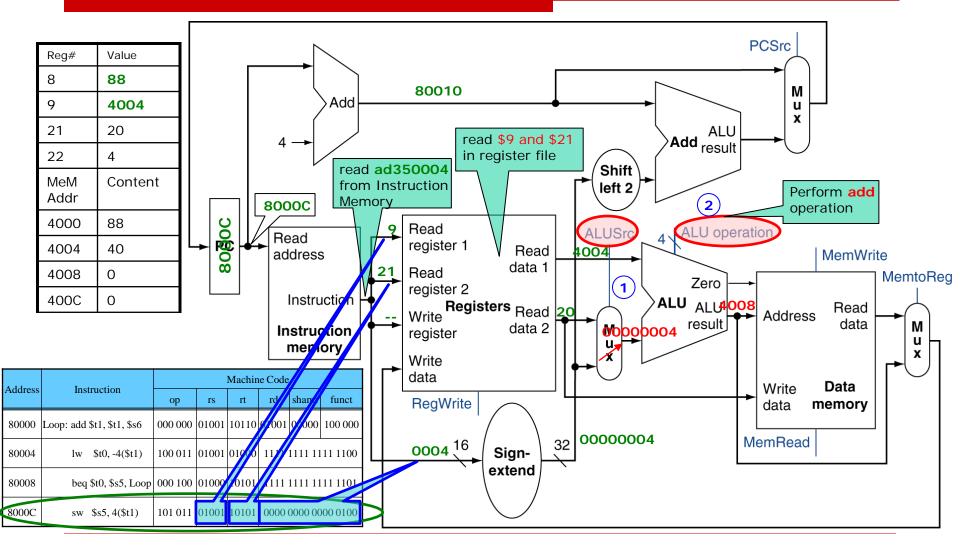
#### How data flow through datapath Example: I-type Instruction: sw (EXE)


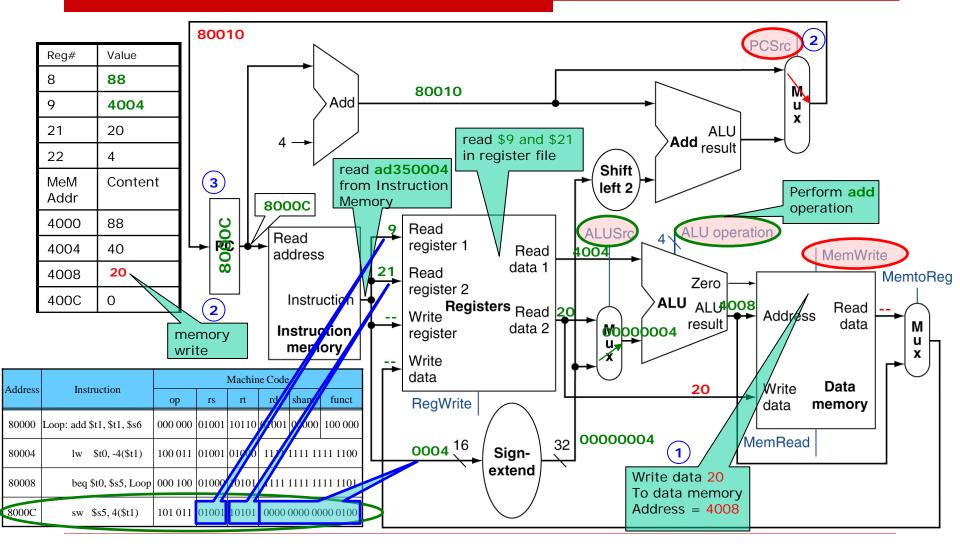
## How data flow through datapath Example: I-type Instruction: sw (MEM)



Chang Gung University