 


EE2011 Computer Organization

Lecture 7: The Processor - Datapath

Wen-Yen Lin, Ph.D.
Department of Electrical Engineering
Chang Gung University
Email: wylin@mail.cgu.edu.tw
May 2022

The Processor: Datapath & Control



The Processor: Datapath & Control

(Ch. 4.1)

- We're ready to look at an implementation of the MIPS
- Simplified to contain only:
 - ⇒ memory-reference instructions: `lw, sw`
 - ⇒ arithmetic-logical instructions: `add, sub, and, or, slt`
 - ⇒ control flow instructions: `beq, j`
- Generic Implementation:
 - ⇒ (PC) to supply instruction address
 - ⇒ get the instruction the program counter action from memory
 - ⇒ read registers
 - ⇒ use the instruction to decide exactly what to do
- All instructions use the ALU after reading the registers
 - Why? memory-reference? arithmetic? control flow?
- After using ALU:
 - ⇒ Memory-reference: access memory for load or store
 - ⇒ Arithmetical-logical: write data from ALU back into register
 - ⇒ Branches: change next instruction address based on comparison

Introduction

- CPU performance factors
 - ⇒ Instruction count
 - Determined by ISA and compiler
 - ⇒ CPI and Cycle time
 - Determined by CPU hardware
- We will examine two MIPS implementations
 - ⇒ A simplified version
 - ⇒ A more realistic pipelined version


Instruction Execution

- PC → instruction memory, fetch instruction
- Register numbers → register file, read registers
- Depending on instruction class
 - ⇒ Use ALU to calculate
 - Arithmetic result
 - Memory address for load/store
 - Branch target address
 - ⇒ Access data memory for load/store
 - ⇒ $PC \leftarrow \text{target address or } PC + 4$

CPU Overview ~

More Implementation Details (Fig. 4.1)


Abstract / Simplified View:

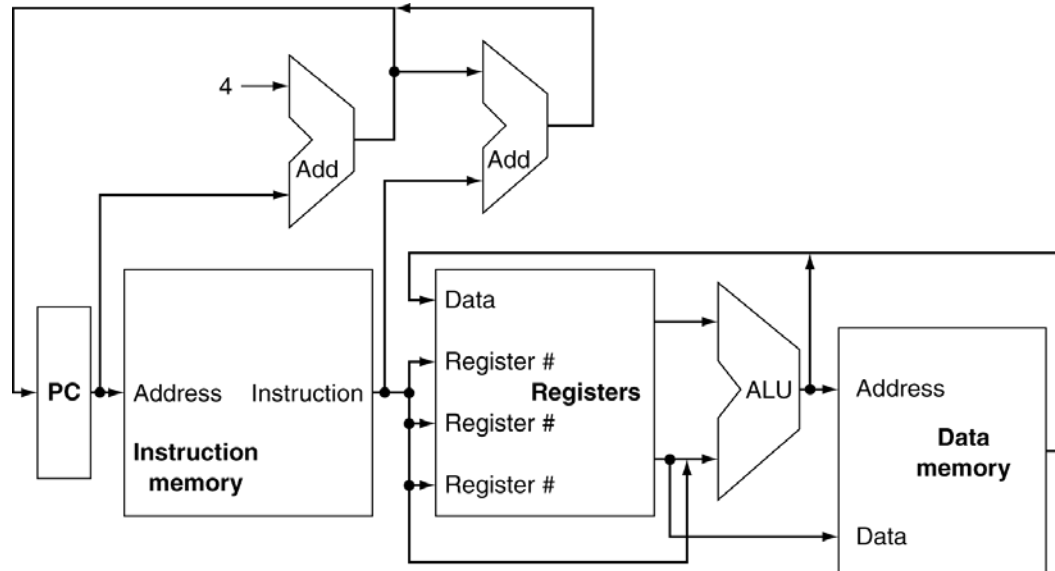

Two types of functional units:


- ⇒ elements that operate on data values (combinational)
- ⇒ elements that contain state (sequential)

Multiplexers

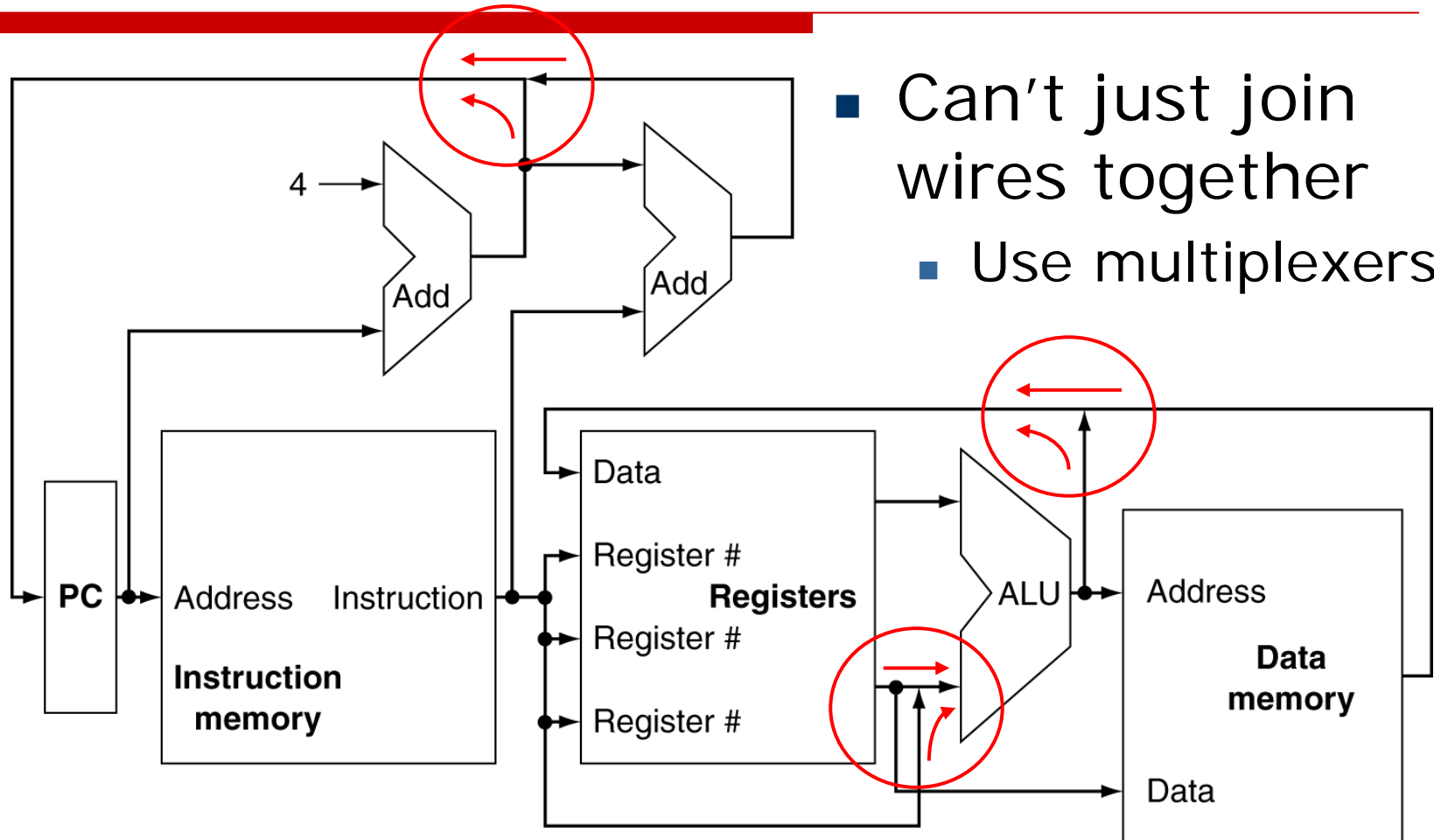

- Can't just join wires together
 - Use multiplexers

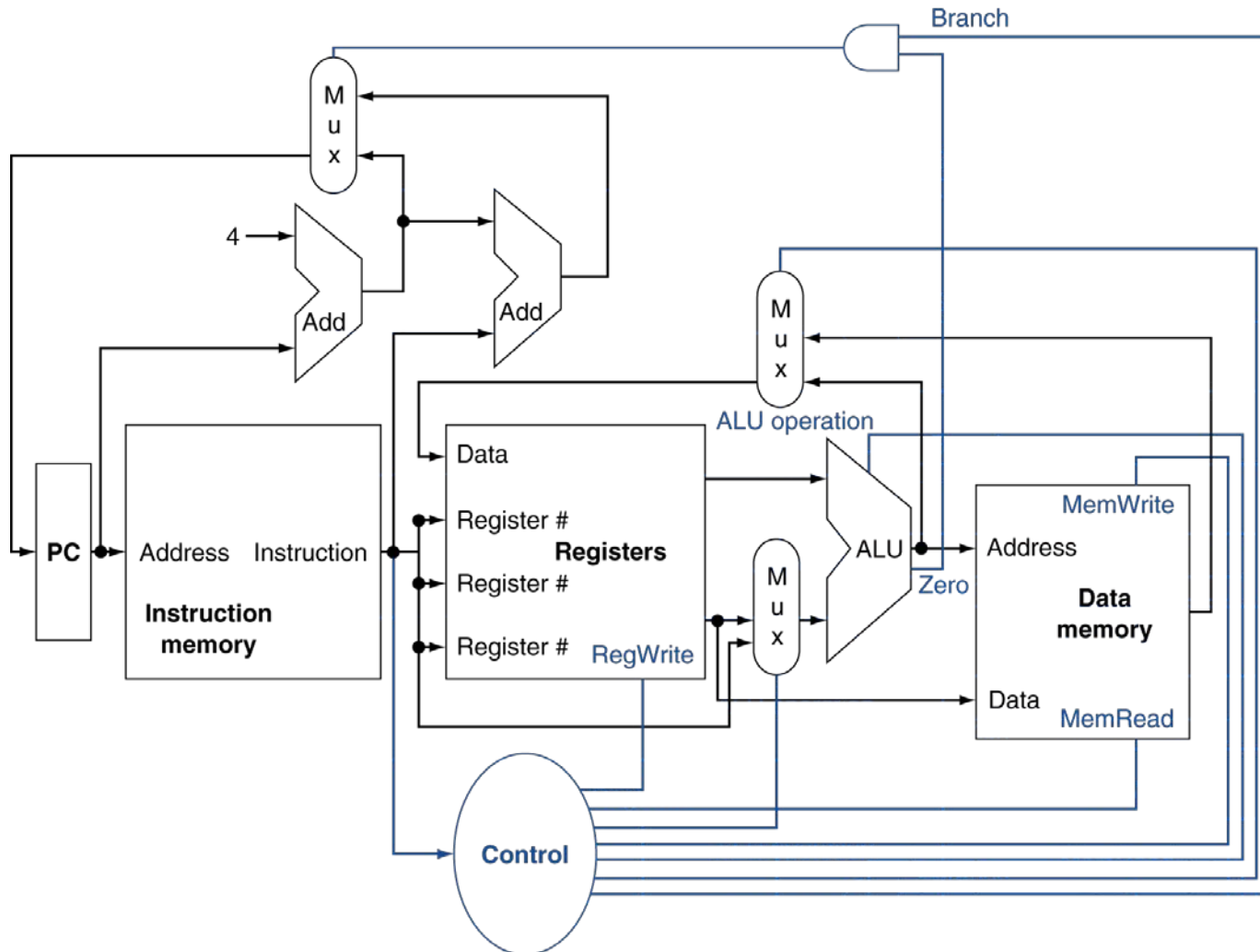Control (Fig. 4.2, To be discussed later ...)




Logic Design Conventions (Ch. 4.2)

- Two types of logic elements in MIPS functional units
 - ⇒ **Combinational**: elements that operate on data values
 - ⇒ **State or sequential**: elements that contain state
 - A synchronous state element has at least
 - Two inputs
 - Data: value to be written
 - Clock: determining when the data value is written
 - One output:
 - Value that was written in an earlier clock cycle

State Elements

 
- Unclocked/Asynchronous vs. Clocked/Synchronous
- Clocks used in synchronous logic
 - ⇒ when should an element that contains state be updated?



An Unclocked/Asynchronous state element

■ The set-reset latch

 - ⇒ output depends on present inputs and also on past inputs (feedbacks)



Clocking Methodology (p. 261)

- Defines when signals can be read and written.
 - ⇒ Additional **control signals** may required to direct the operations, e.g. write enable, etc.

- **Edge-triggered clocking**
 - ⇒ Any values stored in the sequential logic elements are updated only on a **clock edge**

- **Non-edge triggered clocking**
 - ⇒ Any values stored in the sequential logic elements are updated when clock is **asserted**.

- **Combinational logic**
 - ⇒ Has its inputs coming from a set of state elements and its outputs written into a set of state elements
 - ⇒ The inputs are values that were written in a previous clock cycle, while the outputs are values that can be used in following clock cycle.

Latches and Flip-flops

- Output is equal to the stored value inside the element (don't need to ask for permission to look at the value)
- Change of state (value) is based on the clock
- Latches: whenever the inputs change, and the clock is asserted
- Flip-flop: state changes only on a clock edge (edge-triggered methodology)



"logically true",
— could mean electrically low



**A clocking methodology defines when signals can be read and written
— wouldn't want to read a signal at the same time it was being written**


D-latch

  - Two inputs:
 - ⇒ the data value to be stored (D)
 - ⇒ the clock signal (C) indicating when to read & store D
- Two outputs:
 - ⇒ the value of the internal state (Q) and it's complement



D flip-flop


- Output changes only on the clock edge

 

Our Implementation

(Fig. 4.3 & Fig. 4.4)

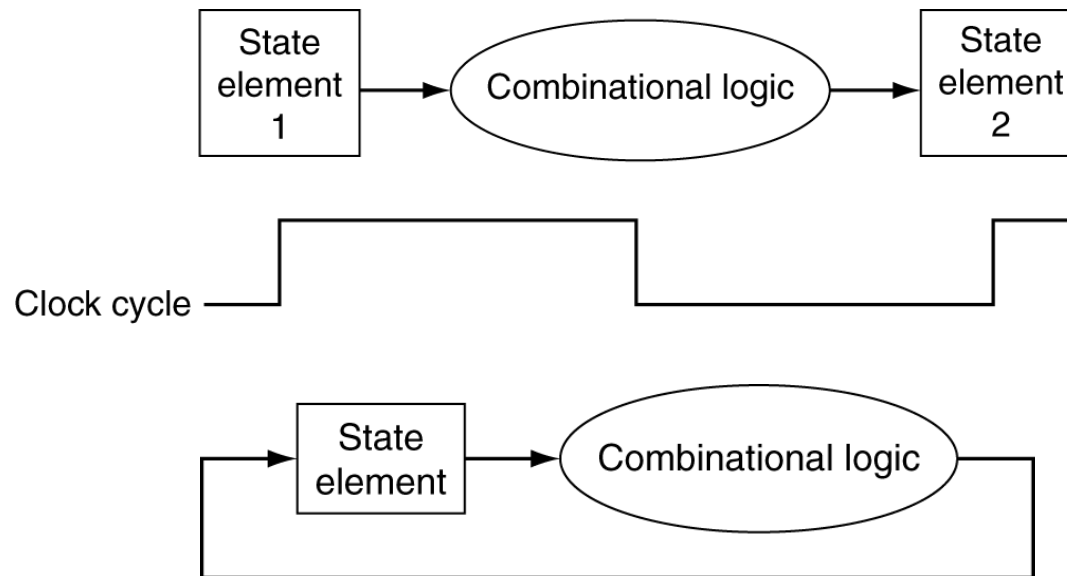- An edge triggered methodology
- Typical execution:
 - ⇒ read contents of some state elements,
 - ⇒ send values through some combinational logic
 - ⇒ write results to one or more state elements



Building a Datapath (Ch. 4.3)



Datapath

- ⇒ Elements that process data and addresses in the CPU
 - Registers, ALUs, mux's, memories, ...



We will build a MIPS datapath incrementally

- ⇒ Refining the overview design

Simple Implementation

Include the functional units we need for each instruction

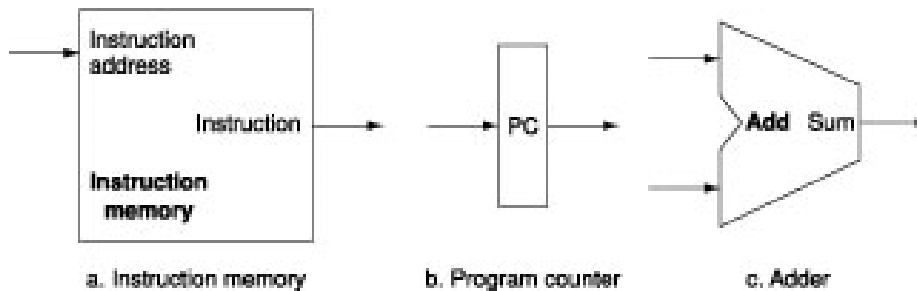


Figure 4.5 Instruction Fetching

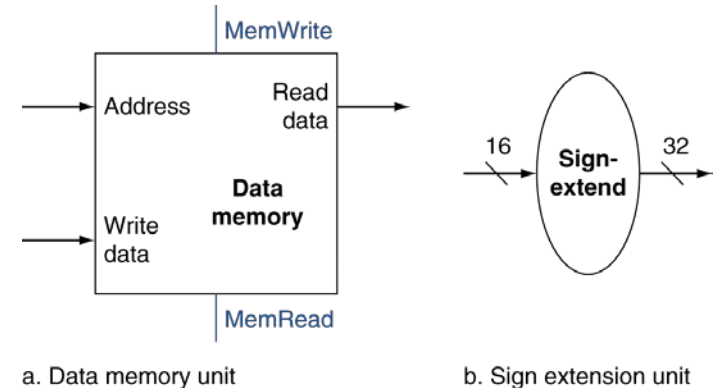


Figure 4.8 Load and Store operations

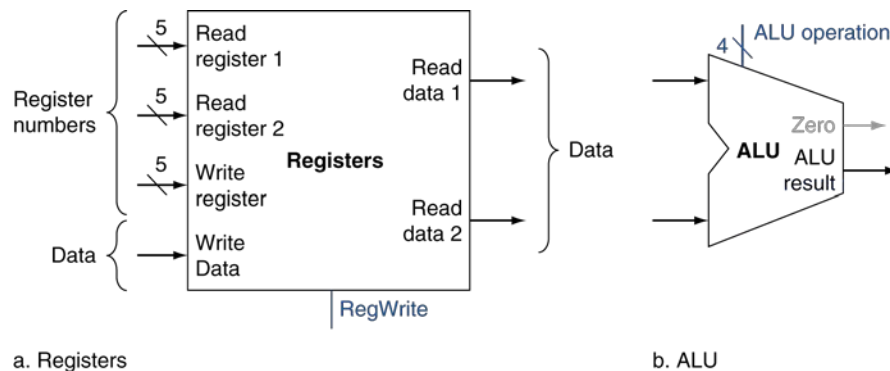


Figure 4.7 R-format ALU operations

Why do we need this stuff?

Building a Datapath

■ The major components required to execute each class of instructions

⇒ **Instruction memory**


- A state element, storing the instructions of a program
- Holds and supplies instructions given an address

⇒ **Program counter (PC)**

- A state element
- Keeps the address of the instruction being executed


⇒ **Adder**

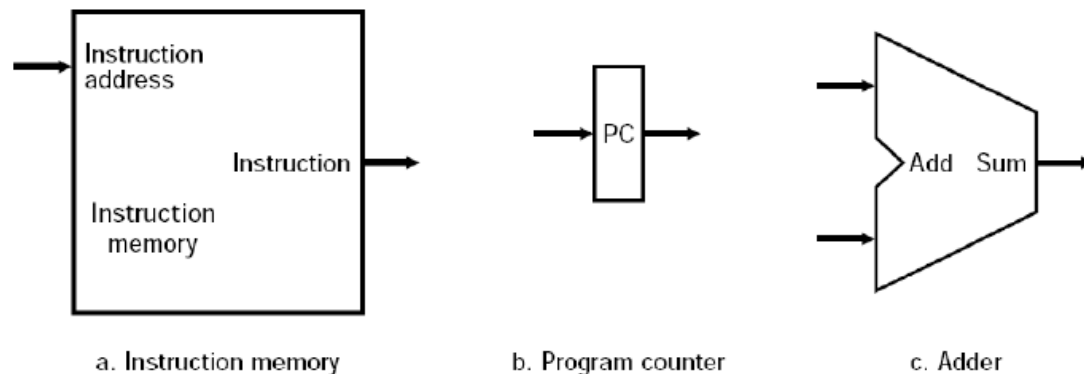- Combinational element
- Increments the PC to the address of the next instruction
- Can be built from the ALU by wiring the control lines




Instruction Fetching (Fig. 4.6)

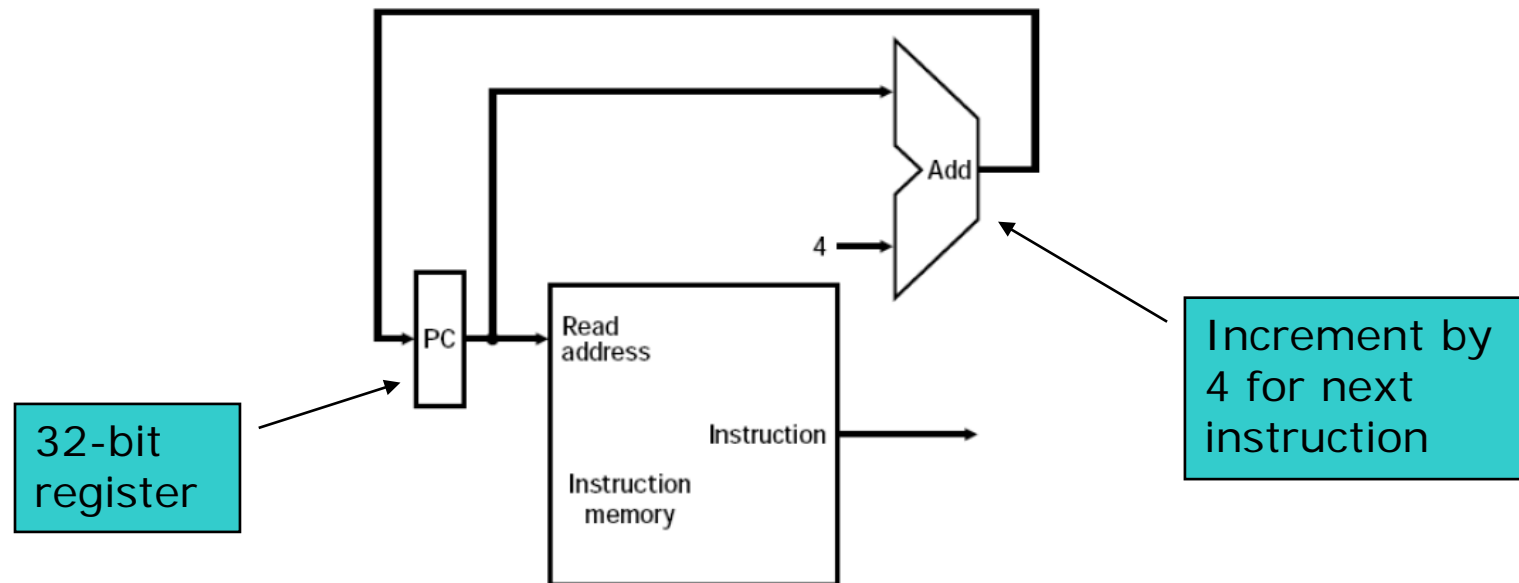- To execute an instruction, start by
 - ➡ Fetching the instruction from memory.
 - ➡ Incrementing PC to point to the next instruction, 4 bytes after.



R-Format Instructions (Fig. 4.7)

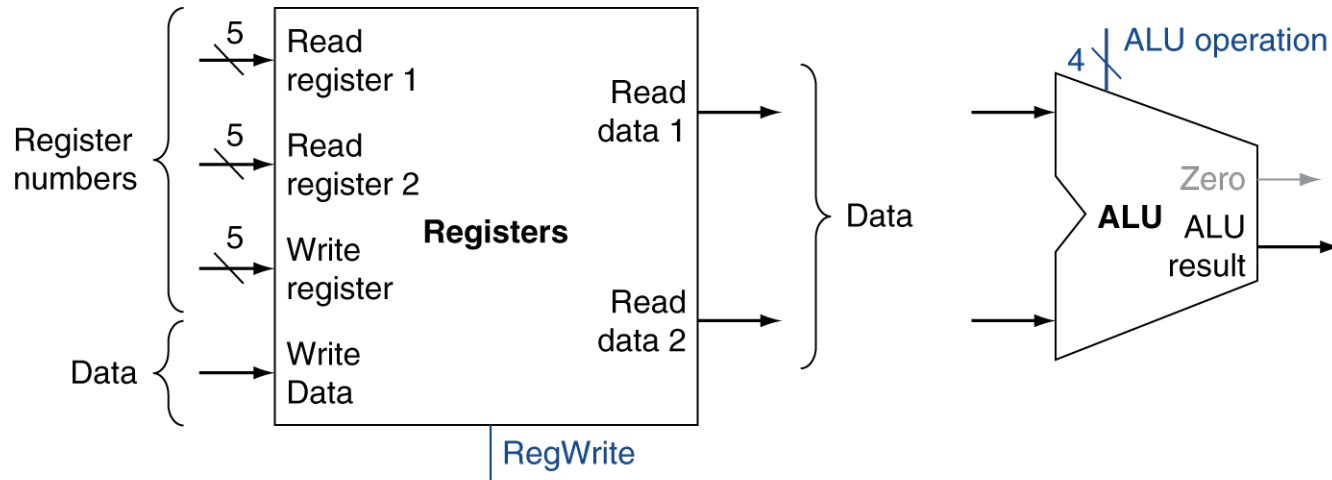- Read two register operands
- Perform arithmetic/logical operation
- Write register result





Name	Fields						Comments
Field size	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits	32 bits
R-format	op	rs	rt	rd	shamt	funct	Arithmetic instruction

Register files (p. 264)

- A collection of 32 **32-bit registers** in which any register can be read or written by specifying the number of the register.
- For R-format instruction, we have to read two data words from, and write one data word into the register file.
- To read a word from the register file, we need
 - ⇒ An input to specify the register number to be read.
 - ⇒ An output to carry the value that has been read.
- To write a word into the register file, we need
 - ⇒ An input to specify the register number to be written
 - ⇒ Any input to supply the data to be written.

Register File Implementation - Read



Built using D flip-flops

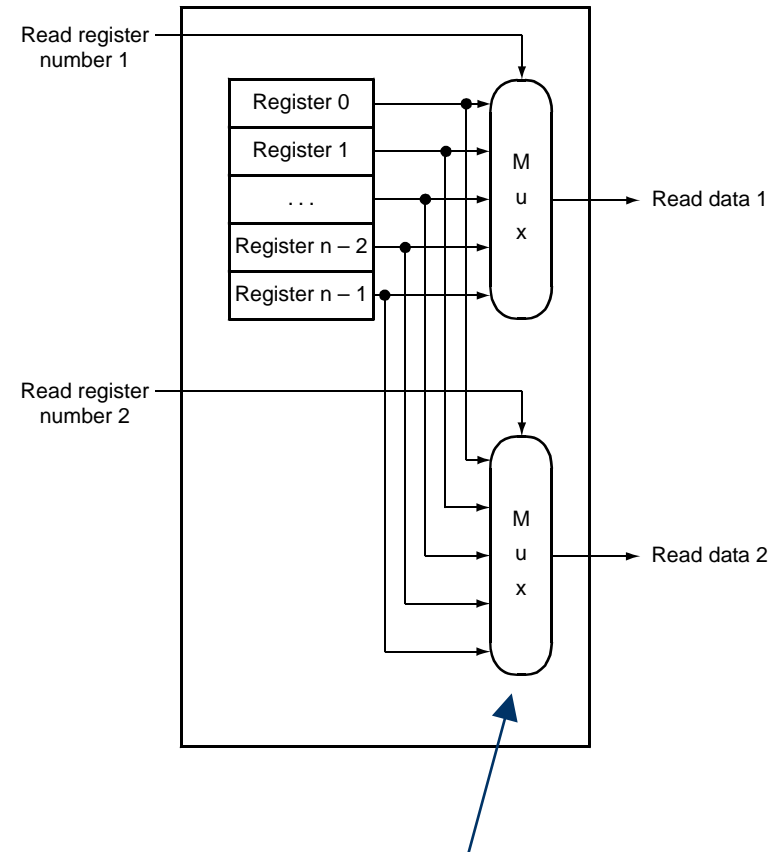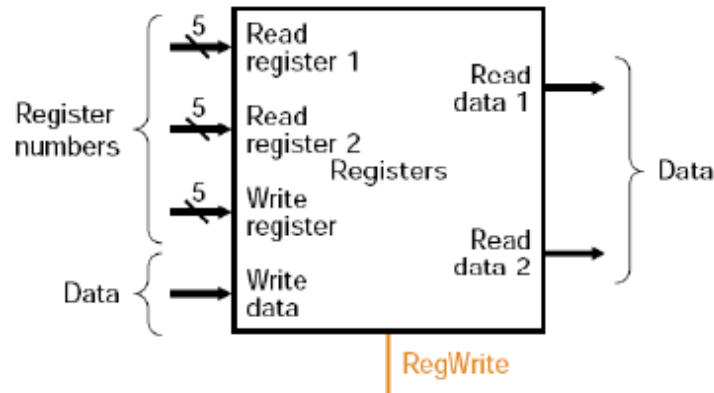

Do you understand? What is the “Mux” above?


Abstraction

  - Make sure you understand the abstractions!
- Sometimes it is easy to think you do, when you don't




Register File Implementation - Write

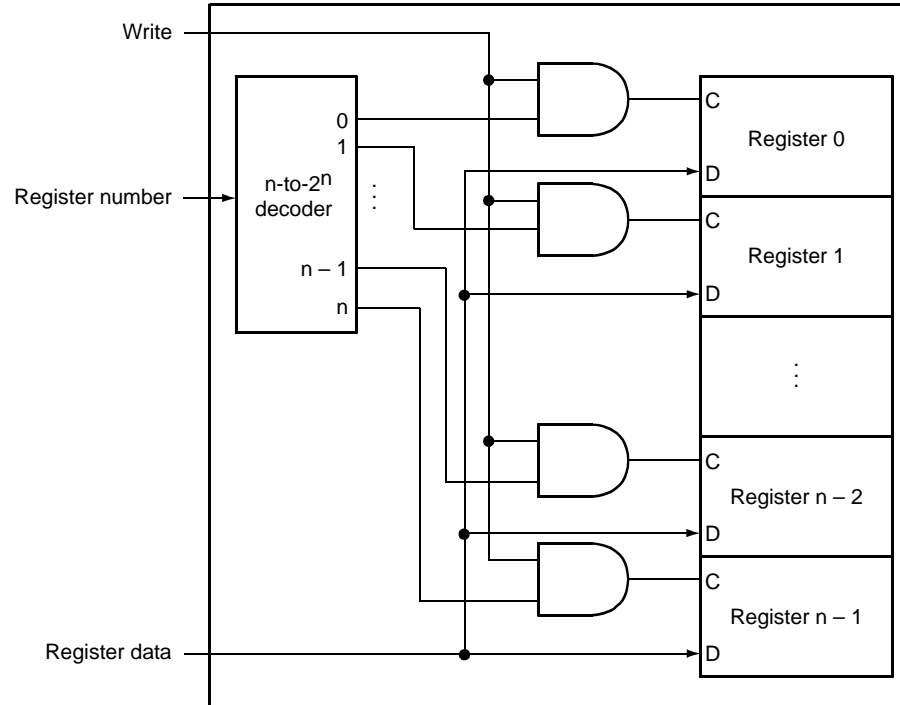- Note: we still use the real clock to determine when to write



Datapath for R-format Instructions

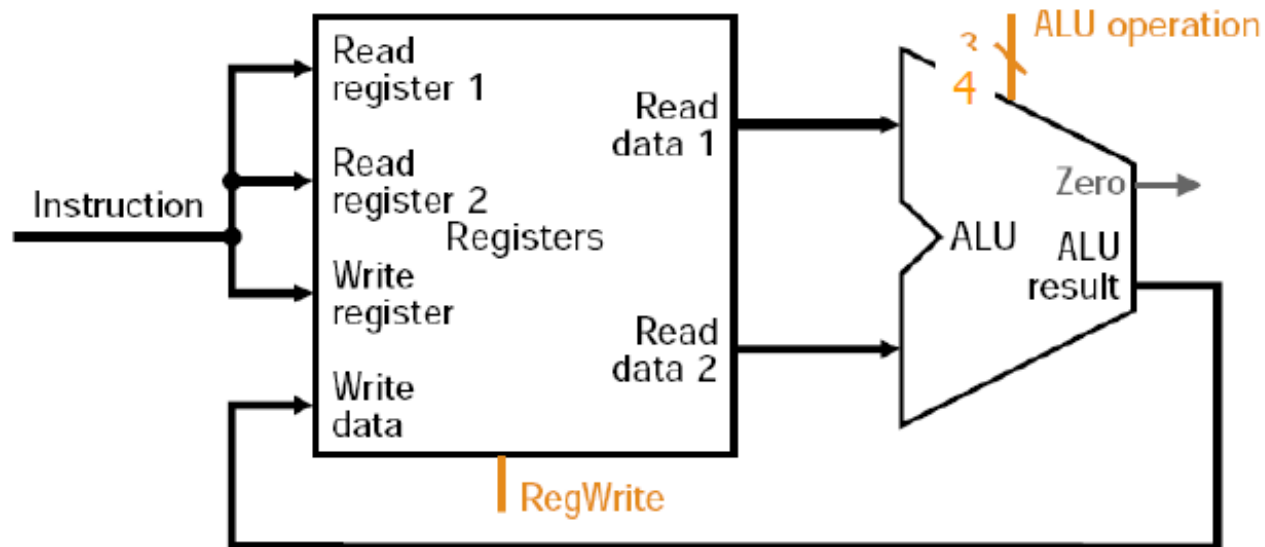

Name	Fields					
Field size	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits
R-format	op	rs	rt	rd	shamt	funct

I-format Instructions – Load & Store



I-format instructions


- ⇒ Load: lw rt, offset(rs)
- ⇒ Store: sw rt, offset(rs)
- ⇒ The memory address is obtained by adding the base register, rs, to the 16-bit signed offset field.

Name	Fields						Comments
Field size	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits	32 bits
I-format	op	rs	rt	address/immediate			Transfer, branch, imm.


Data Memory and Sign-Extension Units

- Data memory unit
 - ⇒ A state element to read from (load) or write to (store)
 - ⇒ Edge-triggered for writes

 - Sign-extension unit
 - ⇒ Combinational element, to sign-extend the 16-bit offset field to a 32-bit signed value




a. Data memory unit

 

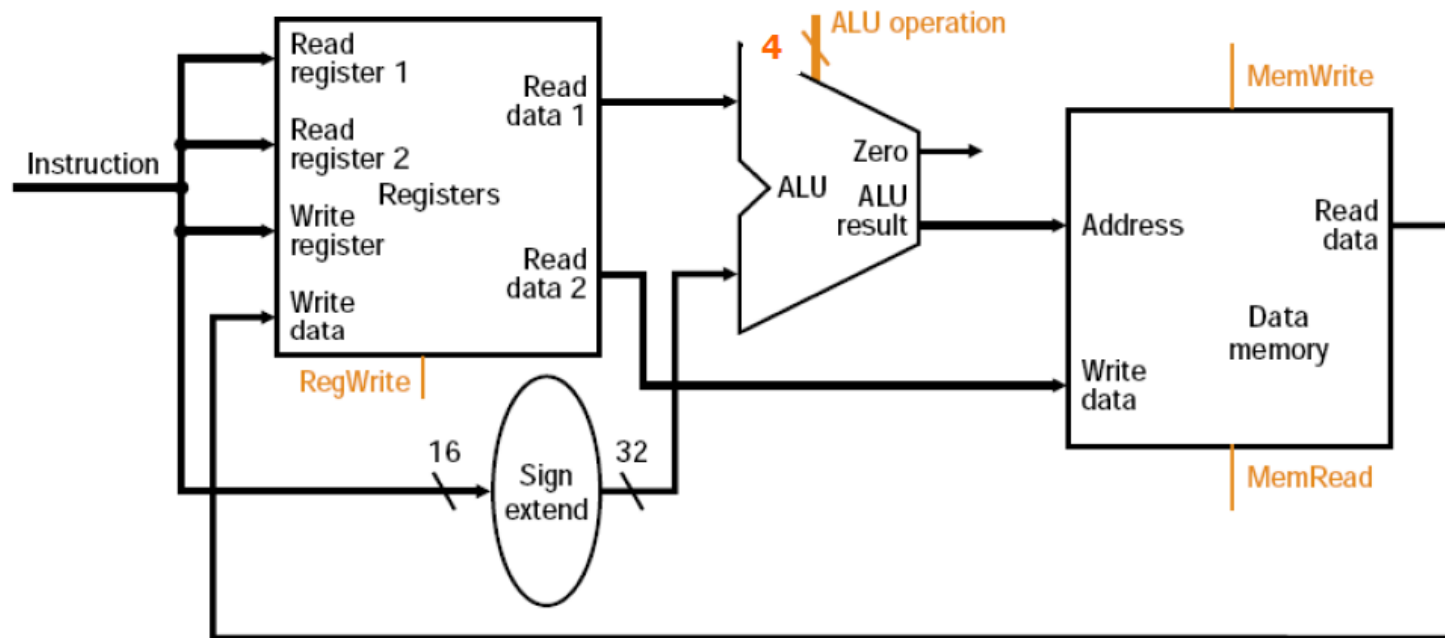b. Sign-extension unit

Datapath for I-format Instructions (Fig. 4.10)



Name	Fields					
Field size	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits
I-format	op	rs	rt	address/immediate		

I-format Instructions – Branch

(p. 266)

- beq rs, rt, offset
 - ⇒ Two registers are compared for equality
 - ⇒ A 16-bit offset is used to compute the **branch target address** relative to the **PC**
- Two details about branch instructions
 - ⇒ The **base** for the branch address calculation is the address of the instruction following the branch instruction, i.e. **PC+4**
 - ⇒ The **offset** is shifted left 2 bits to convert to a **byte offset**.

Name	Fields					
Field size	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits
I-format	op	rs	rt	address/immediate		


Branch Datapath

- Two operations for the branch datapath
 - ⇒ Compute the branch target address
 - ⇒ Compare the register contents

- To perform the compare
 - ⇒ Set the ALU operation to subtraction
 - ⇒ Decide if the two register contents are equal by **zero** output

- If the condition is
 - ⇒ True (**branch taken**): the branch target address becomes the new PC
 - ⇒ Not True (**branch not taken**): the incremented PC replaces the current PC.

Branch Datapath (Fig. 4.9)

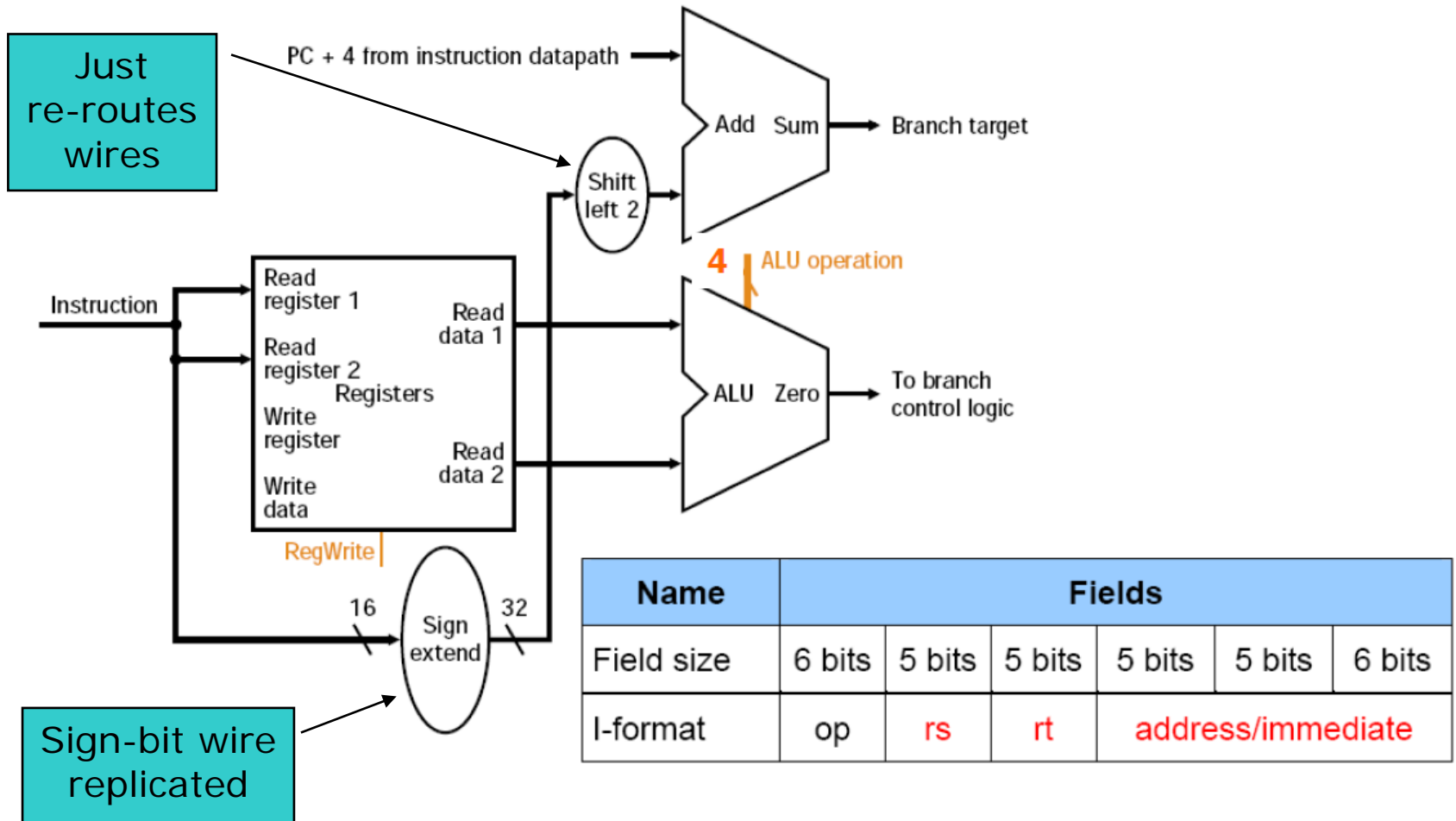

J-Format Instructions - Jump

- Replace the lower 28 bits of the PC with the lower 26 bits of the instruction shifted left by 2 bits (word address to byte address)
- Leave the upper 4 bits of the PC unchanged.

Name	Fields						Comments
Field size	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits	32 bits
J-format	op	target address					Jump instruction

Composing the Elements (p. 268)


- First-cut data path does an instruction in one clock cycle
 - ⇒ Each datapath element can only do one function at a time
 - ⇒ Hence, we need separate instruction and data memories
- Use multiplexers where alternate data sources are used for different instructions

Single-Cycle Datapath


- All instructions are executed in **one** clock cycle.
- No datapath resource can be used more than once per instruction
- An element needed more than once must be duplicated
 - ⇒ Two memories: one for **instruction** and one for **data**
- Some functional units can be shared by different instructions
 - ⇒ We need to allow multiple connections to the input of an element and have a control signal select among the inputs.
 - ⇒ The selection is commonly done with a multiplexor

R-Type/Load/Store Datapath (Fig. 4.10)

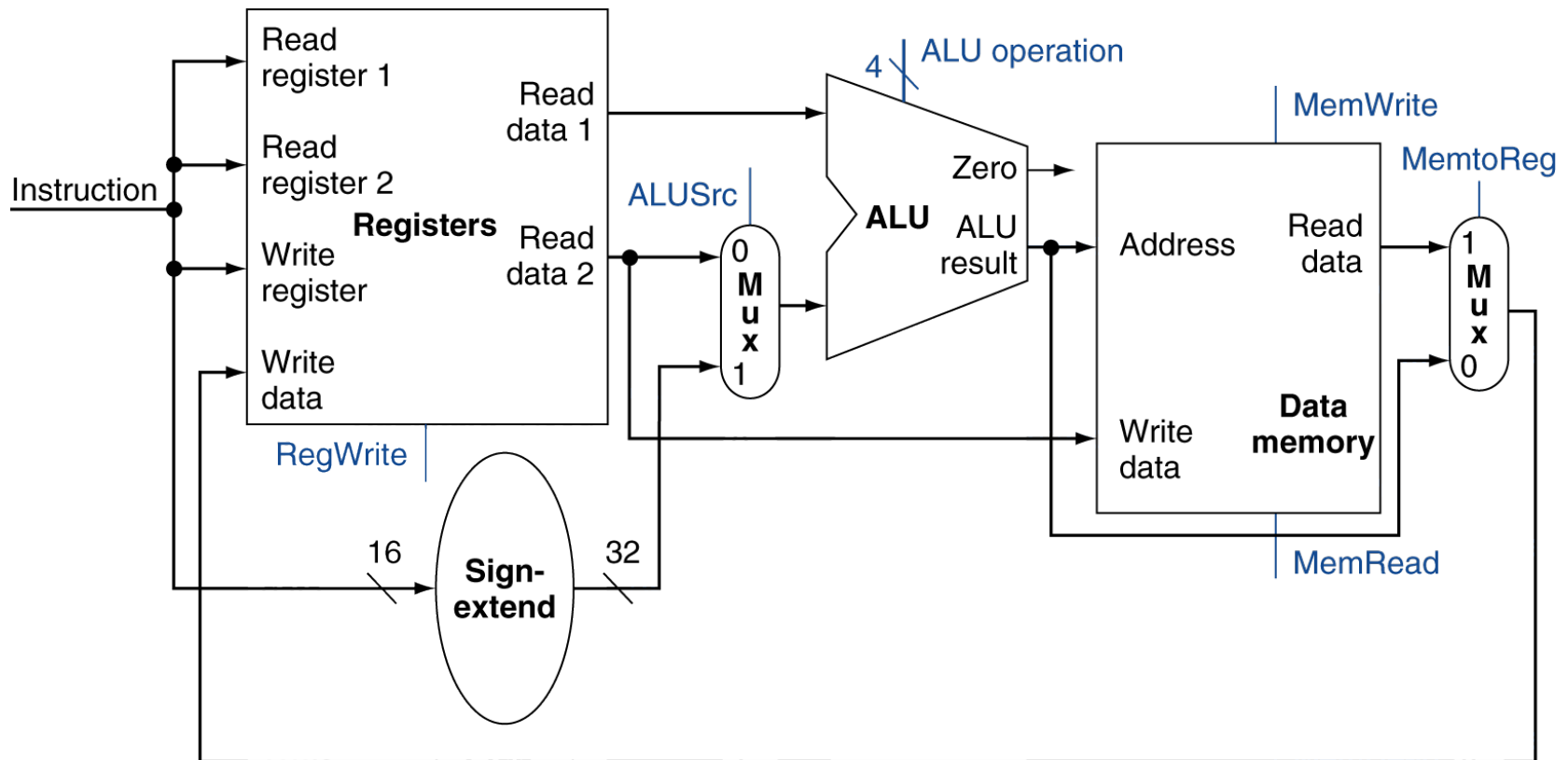
- Use multiplexers to stitch them together




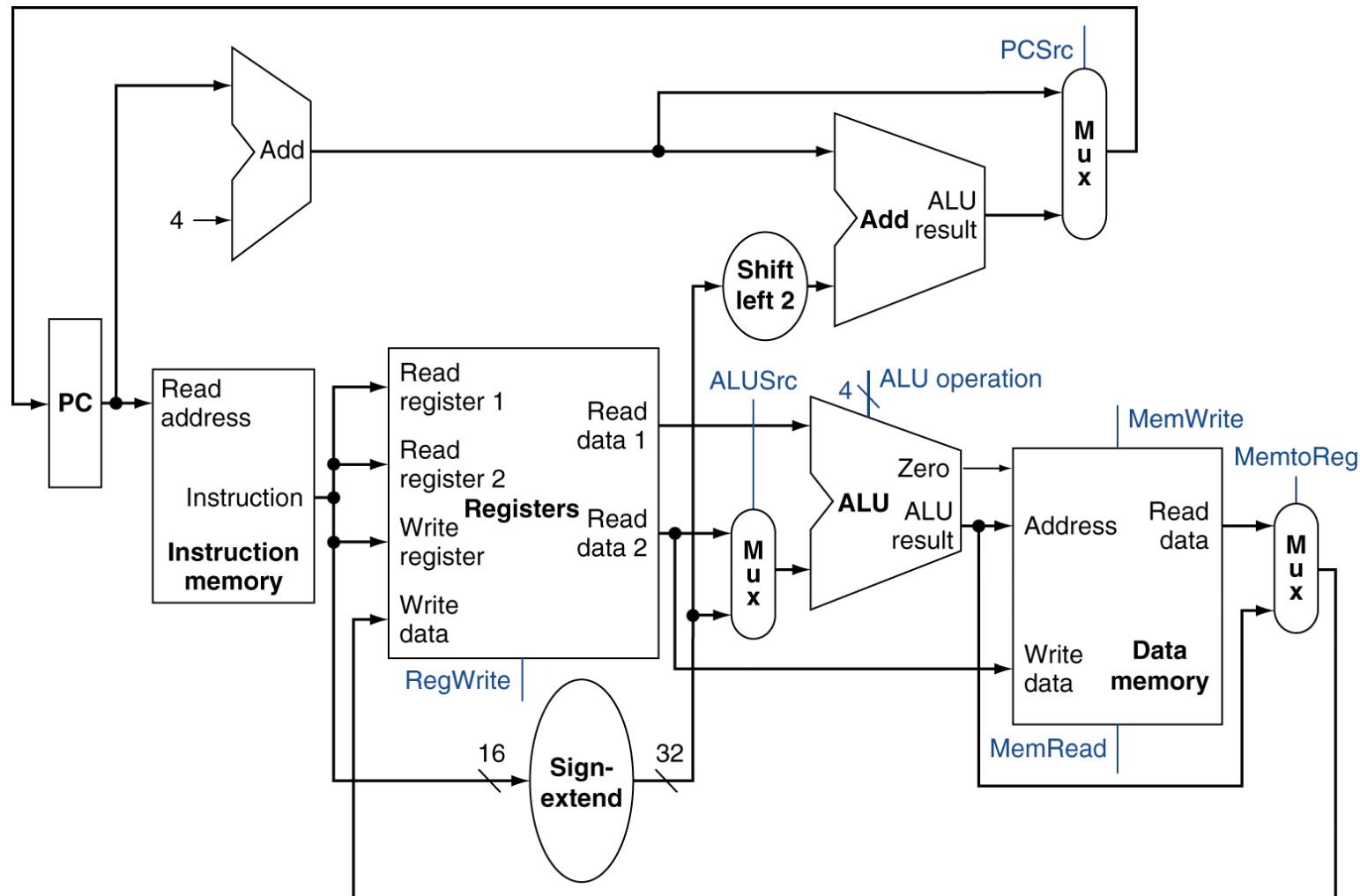Putting All Together for the Datapath (Fig. 4.11)



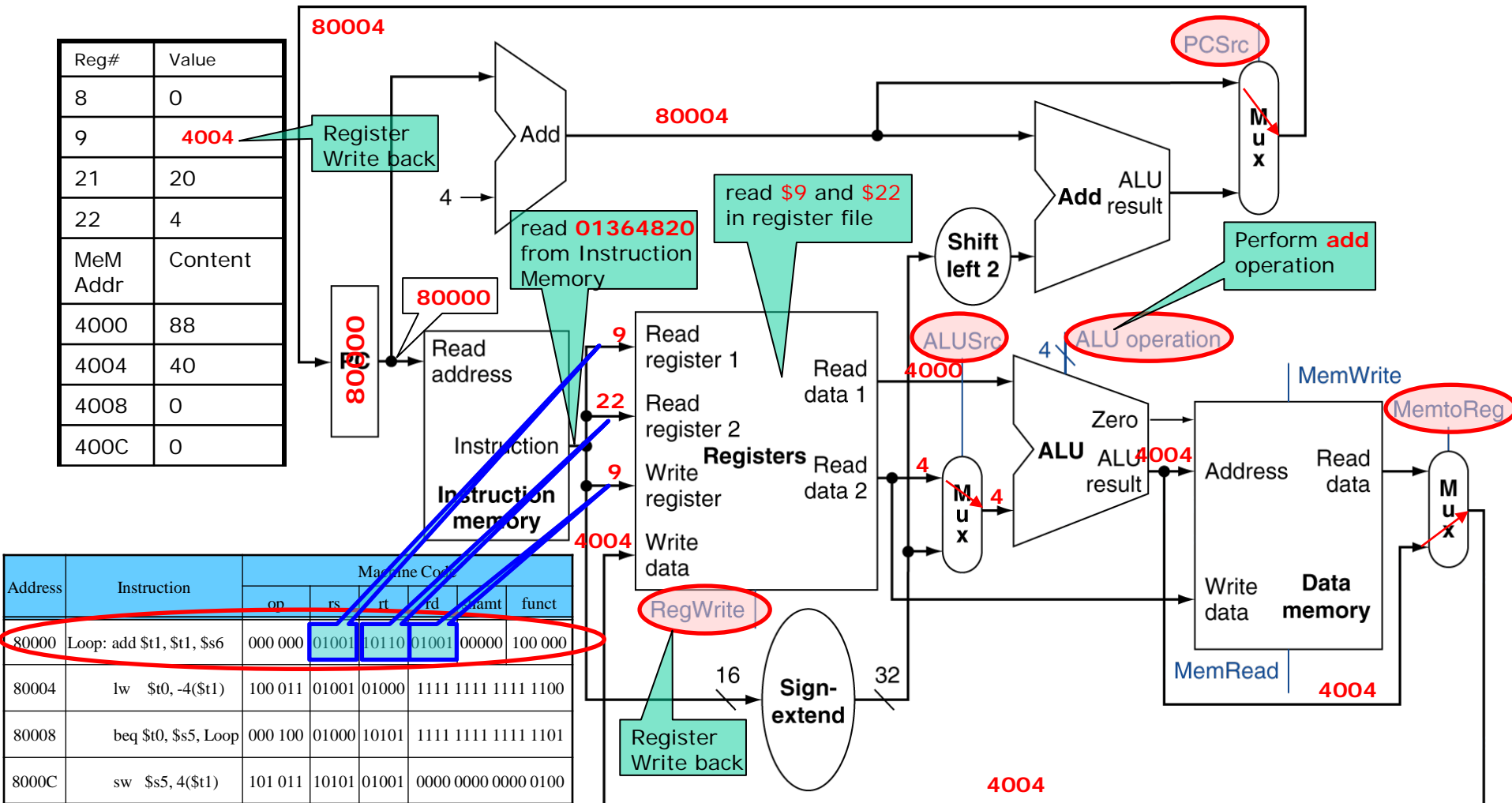Example ~ How data flow through datapath (R-type Instruction: Add)



 



Example ~ How data flow through datapath (I-type Instruction: sw)

